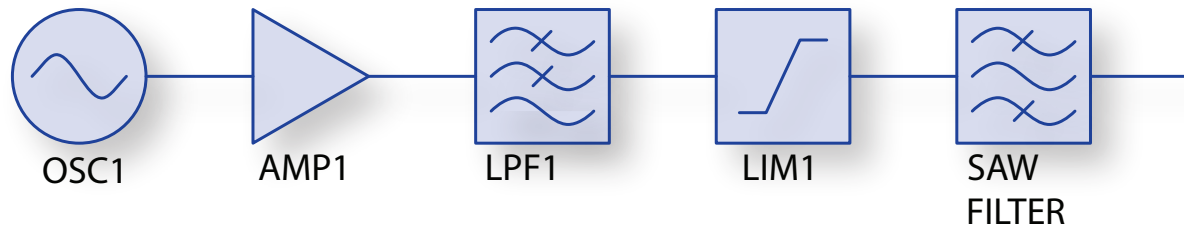


# X7 MULTIPLIER



| Schematic Part No. | Sample Mini-Circuits Model Families   |
|--------------------|---|
| AMP1               | <a href="#">ERA</a> , <a href="#">GVA</a> , <a href="#">MAR</a> , <a href="#">GALI</a> , <a href="#">VNA</a> , <a href="#">VAM</a> , <a href="#">RAM</a> , <a href="#">YSF</a> , <a href="#">MNA</a> ,<br><a href="#">LEE</a> , <a href="#">PGA</a> , <a href="#">PHA</a> , <a href="#">PSA</a> |
| LIM1               | <a href="#">RLM</a>   |
| LPF1               | <a href="#">LFCN</a> , <a href="#">XLF</a> , <a href="#">LFCW</a> , <a href="#">LFTC</a> , <a href="#">LPE</a> , <a href="#">RLP</a> , <a href="#">SALF</a> , <a href="#">SCLF</a> , <a href="#">SXLP</a>   |
| OSC1               | <a href="#">ROS</a> , <a href="#">KOS</a> , <a href="#">KSN</a>   |